

Chapter–3

Current Electricity



CBSE CLASS XII NOTES

Dr. SIMIL RAHMAN


MSc,Ph.D,B.Ed,

D.E.E.I Engineering,SET,MA

MES DOHA QATAR



cell

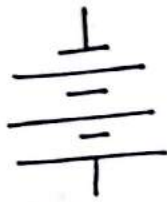

Battery



switch



key



voltmeter



Ammeter



galvanometer




Resistor



variable resistor



Bulb

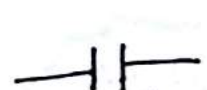

capacitor



variable capacitor

best of luck

Thank you

For more information

visit our website

www.learnerslab.com

or call us at 0800 123 4567

Electric current

Rate of flow of charge

$$I = \frac{q}{t}$$

S.I unit - Ampere.

conventional current

opposite to the flow of electrons

Electromotive force [EMF]

amount of work done by a source to move unit charge around a complete circuit.

current density (j)

$$j = \frac{\text{current}}{\text{unit area}}$$

$$j = \frac{I}{A}, \text{ S.I unit } A/m^2$$

→ vector quantity
→ Direction is along \vec{E} .

How electrons are drifted in an Electric field?

In the absence of Electric field

Average velocity of $\bar{e} = 0$ (due to random motion)

In the presence of Electric field

\bar{e} ns are accelerated

$$F = ma = qE$$

$$\{q = -e\}$$

$$ma = -eE$$

$$\therefore a = -\frac{eE}{m}$$

Thus they get scattered due to collision.

relaxation time (τ)


average time interval between successive collisions of \bar{e} .

Drift velocity

average velocity with which free \bar{e} 's get drifted under the influence of an \vec{E} .

$$\vec{v}_d = -\frac{e\vec{E}\tau}{m}$$

$\vec{v}_d \rightarrow$ drift velocity.

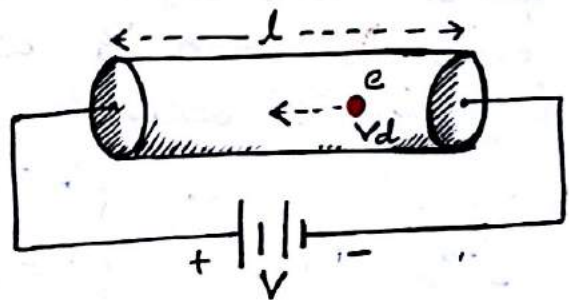

when an electric field \vec{E} is applied, the \bar{e} 's modify their speed in such a way that they drift slowly in the direction opposite to that of field.

$$F = ma = qE = -eE$$

$$ma = -eE$$

$$a = -\frac{eE}{m}$$

$$V = u + at$$

$$V = 0 + at = at \quad \dots \textcircled{1}$$

here $V = \vec{v}_d$ & $t = \tau$


$\therefore \textcircled{1} \Rightarrow$

$$\vec{v}_d = -\frac{eE}{m} \tau$$

$$v_d = \frac{eE\tau}{m}$$

'-' sign indicates \vec{v}_d is opposite to \vec{E} .

Relation between current and v_d

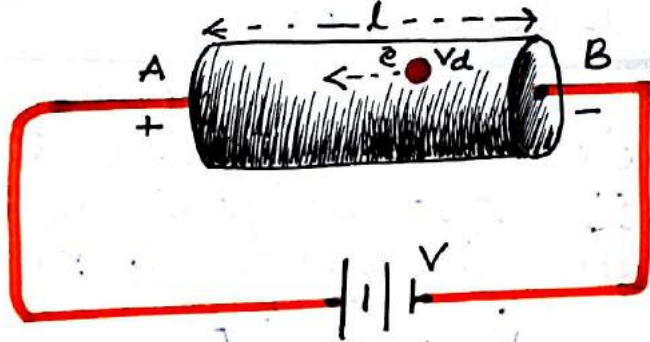

Let 'q' charges pass through cross sectional area 'A' of the wire in 't' seconds.


$$t = \frac{l}{v_d}$$

$$v = \frac{s}{t} \implies t = \frac{s}{v}$$

$n = \frac{\text{No of } e's}{\text{unit volume}}$

here $t = \frac{l}{v_d}$

$$n = \frac{N}{Al}$$

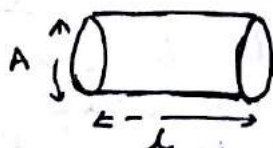

Volume = Al

$$N = nAl$$

$$\text{charge } q = Ne = nAl e$$

$$\text{current } I = \frac{q}{t}$$

$$I = \frac{Ne}{t} = \frac{nAl e}{t} \quad \dots \textcircled{1}$$

since $t = \frac{l}{v_d}$

$$\textcircled{1} \Rightarrow I = \frac{nAl e}{\frac{l}{v_d}} = nAe v_d$$

$$I = nAe v_d$$

$$I = nAe v_d$$

Relation b/w current density and relaxation time

$$I = nAe v_d$$

$$j = \frac{I}{A} = \frac{nAe v_d}{A} = ne v_d$$

$$\therefore j = ne v_d \implies v_d = \frac{eE\tau}{m}$$

$$j = ne \left(\frac{eE\tau}{m} \right)$$

$$j = \frac{ne^2 E \tau}{m}$$

Mobility (μ), electron mobility or ionic mobility

mobility = $\frac{\text{drift velocity}}{\text{unit electric field}}$

$$\mu = \frac{|v_d|}{E} = \frac{eE\tau}{mE} = \frac{e\tau}{m}$$

$$\text{S.I unit} = \left(\frac{ms^{-1}}{Vm^{-1}} \right) = m^2/Vs$$

relation b/w μ & τ (mobility & Relaxation time)

$$\mu = \frac{Vd}{E} = \frac{eE\tau}{mE} = \frac{e\tau}{m}$$

$$\mu = \frac{e}{m} \tau$$


Ohm's Law.

At constant temperature current is directly proportional to the potential difference between ends of a conductor.

$$V \propto I$$

$$V = IR$$

$$\frac{V}{I} = R = \text{const}$$

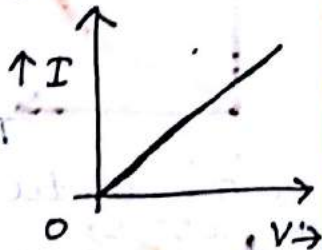

* If temp changes Ohm's law doesn't hold good because 'R' changes.

* unit of Resistance - Ω (ohm)

Factors affecting resistance.

- (1) Nature of material
- (2) length of conductor
- (3) Area of cross section of conductor.

4, Temperature

ie, $R \propto l$, ~~$R \propto l$~~ , $R \propto \frac{l}{A}$

$$\therefore R \propto \frac{l}{A}$$

$$R = \rho \frac{l}{A}$$

$\rho \rightarrow$ Resistivity

Resistivity (ρ)

Resistivity of a conductor can be defined as the resistance of the conductor of unit length and unit area of cross section.

ie, $\rho = \frac{RA}{l}$.. $R = \frac{\rho l}{A}$

if $l=1$, $A=1$

$$\rho = R$$

SI unit = $\underline{\underline{\Omega m}}$

Conductivity σ

Reciprocal of resistivity is conductivity

$$\sigma = \frac{1}{\rho}$$

SI unit - $\Omega^{-1} m^{-1}$ or $S m^{-1}$

[mho/metre]

Relationship between E and ρ , j and σ

$$V = IR = I \frac{\rho l}{A}$$

$$V = I \rho \frac{l}{A}$$

$$E l = \frac{I \rho l}{A}$$

$$E = \frac{I \rho}{A}$$

$$E = j \rho$$

$$\therefore j = E / \rho$$

$$j = \sigma E$$

$$V = E d$$

here $d = l$

$$V = E \cdot l$$

$$j = \frac{I}{A}$$

$$\frac{1}{\rho} = \sigma$$

Resistivity of conductors (metals), Insulators and Semiconductors.

Metals - very low $10^{-8} \Omega m$ to $10^{-6} \Omega m$

Insulators - very high 10^{18} times of that of metals.

Semiconductors - between conductors and Insulators.

Relation b/w ρ, n, τ

$$I = n A e v d$$

$$I = n A e \left(\frac{e E}{m} \right) \tau$$

$$I = n A e^2 \frac{E \tau}{m}$$

$$I = n A e^2 \frac{V \tau}{l m} \quad \text{--- (1)}$$

$$E = \frac{V}{d}$$

$$E = \frac{V}{l}$$

$$\frac{V}{I} = \frac{m l}{n A e^2 \tau}$$

$$\frac{V}{I} = \frac{m l}{n A e^2 \tau} \quad \text{--- (2)}$$



$$R = \frac{m}{n e^2 \tau} \left(\frac{l}{A} \right) \quad \text{--- (2)}$$

but we know that

$$R = \rho \frac{l}{A} \quad \text{--- (3)}$$

$$\therefore (2) \& (3) \Rightarrow \rho = \frac{m}{n e^2 \tau}$$

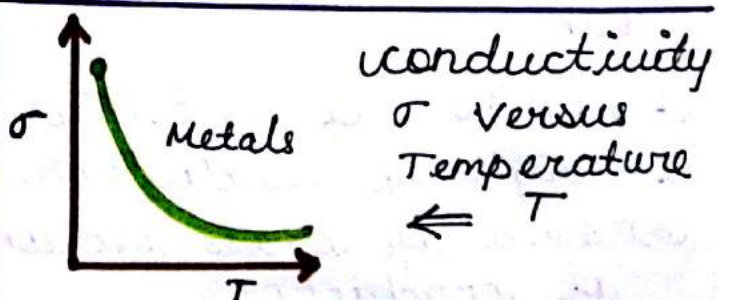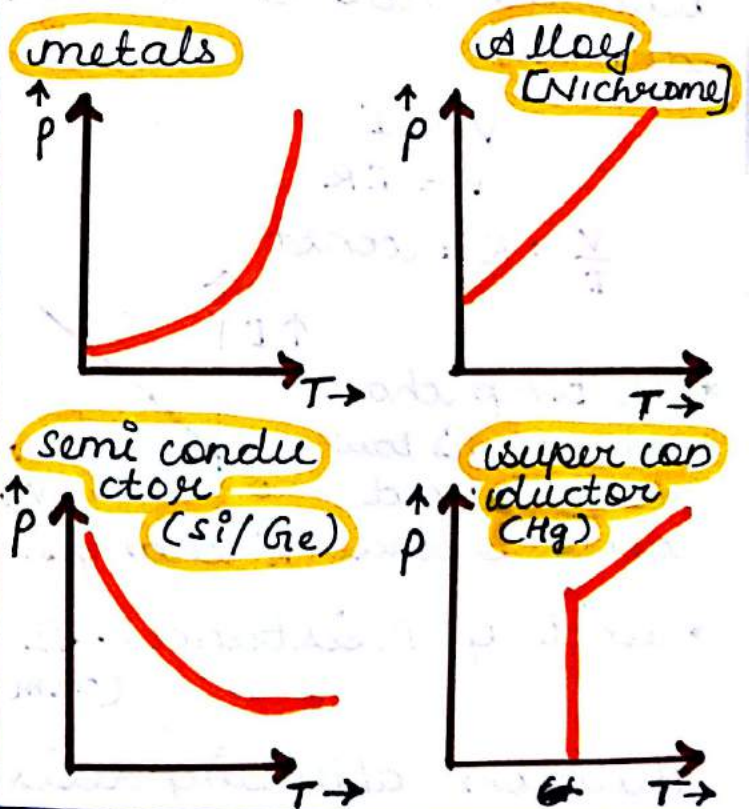Graphical relationship b/w Resistivity (ρ) and Temperature T in Kelvin



conductivity σ versus Temperature T


ohmic and non ohmic conductors

ohmic conductors: obey ohm's law.
eg. Metals


Non ohmic conductors: does not obey ohm's law
eg. Semiconductors.

limitations of ohm's law.

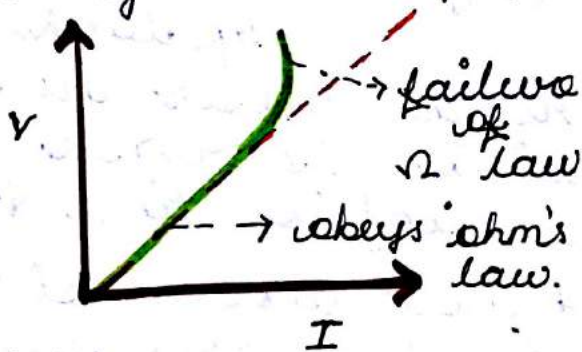
* V-I graph is linear only for small amount of current. when temperature increases we won't get linear graph.



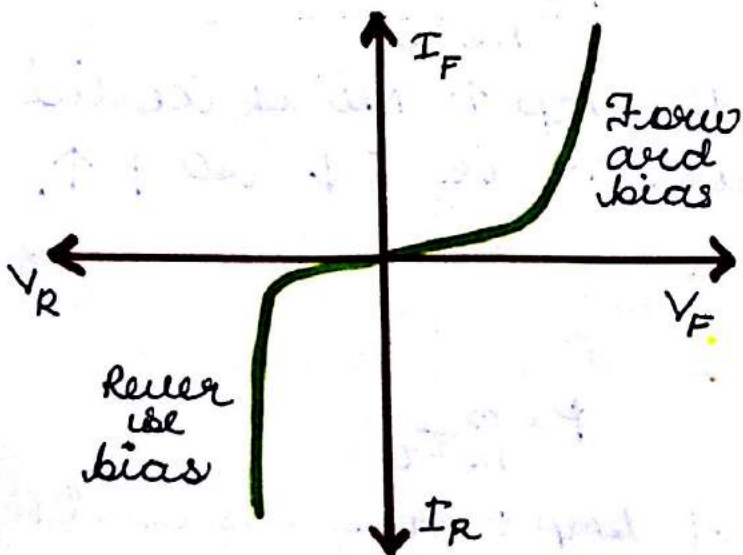* semiconductors do not obey ohm's law (Non-ohmic)



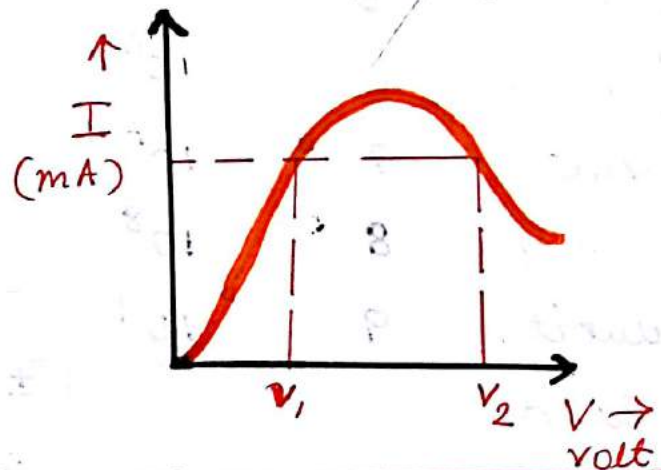* more than one value of voltage for same current in GaAs



Types of resistors

(a) Wire bound resistor.

- * Nichrome, Manganin (alloys) are used
- * Resistances are typically in the range of a fraction of a Ω to few hundred Ω 's.

(b) Carbon resistor.

- * They are compact, inexpensive
- * high value of R
- * smaller in size.
- * colour codes are used.

colour codes of carbon resistor.

colour code	Number	multiplier	Tolerance
Black	0	1	
Brown	1	10^1	
Red	2	10^2	

Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	
Blue	6	10^6	
Violet	7	10^7	
Grey	8	10^8	
White	9	10^9	
Gold			$\pm 5\%$
Silver			$\pm 10\%$
No colour			$\pm 20\%$

* You are required to select a carbon resistor of resistance $47k\Omega \pm 10\%$ from a large collection. What should be the sequence of colour bands used to code it? [F-2011]

$47k\Omega \pm 10\%$
 $47 \times 10^3 \pm 10\%$

↓ silver
 yellow violet, orange
 yellow, violet, orange, silver

How to find R value using colour codes.

- First 2 bands - significant figures
- 3rd band - multiplier
- 4th band - Tolerance

* A carbon resistor is marked in colour bands of red, black, orange and silver. What is the resistance and tolerance value of the resistor? [2002]

Red, Black, 0, Silver
 2 0 3 $\pm 10\%$

$R = 20 \times 10^3 \pm 10\%$
 $R = \underline{\underline{20k\Omega \pm 10\%}}$

* How is relaxation time affected on rising temperature?

If temperature increases no. of collisions increases hence relaxation time \downarrow ($\tau \downarrow$)

* How does resistivity increase when temperature \uparrow in metals?

$$\rho = \frac{m}{ne^2\tau}$$

If temp \uparrow No. of collisions \uparrow i.e., $\tau \downarrow$ so $\rho \uparrow$.

* How does resistivity \downarrow when temperature \uparrow in a semiconductor?

$$\rho = \frac{m}{ne^2\tau}$$

If temp \uparrow no. of free e's $n \uparrow$ & $\tau \uparrow$

Temperature co-efficient (α)

$$\alpha = \frac{R_T - R_0}{R_0 (T - T_0)}$$

if $R_0 = 1, T - T_0 = 1, \alpha = R_T - R_0$

Temperature

co-efficient is the increase in resistance per unit original resistance at 0°C per unit rise in temperature.

compare Temperature coefficient of

- (1) metals
- (2) alloys
- (3) semiconductors.

- (1) metals ' α ' is positive
- (2) alloys ' α ' is positive but very small
- (3) semiconductors ' α ' is negative.

Expressions for ρ and R at a given temperature.

$$\rho_T = \rho_0 [1 + \alpha (T - T_0)]$$

$$\rho_2 = \rho_1 [1 + \alpha (T_2 - T_1)]$$

$$R_T = R_0 [1 + \alpha (T - T_0)]$$

$$R_2 = R_1 [1 + \alpha (T_2 - T_1)]$$

R_T & $\rho_0 \rightarrow R$ at $T^\circ\text{C}$ and 0°C

R_T and $R_0 - R$ at $T^\circ\text{C}$ and 0°C

R_1 and $R_2 - R$ at $T_1^\circ\text{C}$ and $T_2^\circ\text{C}$

Joule's law.

according to

Joule's law.

$$H \propto I^2$$

$$H = I^2 R t$$

$$H = V I t$$

$$H = \frac{V^2}{R} t$$


$$R = \frac{V}{I}$$

$I \rightarrow$ current, $H \rightarrow$ heat energy, $t \rightarrow$ time of flow of current.

Questions

Plot a graph showing the variation of resistance of a conducting wire as a function of its radius, keeping the length of the wire and its temperature as constant? [CBSE (F) 2013]

$$R = \rho \frac{l}{\pi r^2}$$

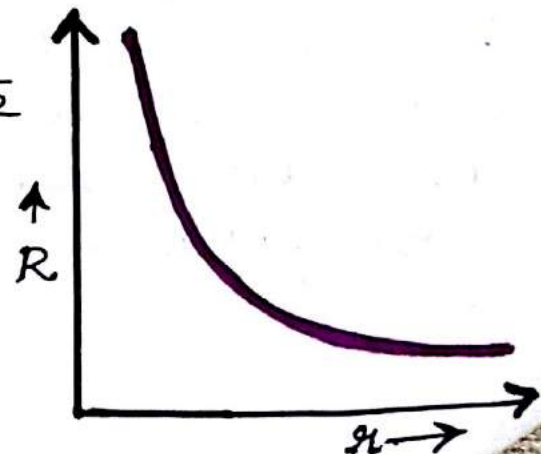


Power / power Transmission

Rate of energy dissipation in a resistor is called the power i.e., power

$$P = \frac{W}{t} = \frac{VI \cdot t}{t} = VI$$

$$P = I^2 R = \frac{V^2}{R}$$

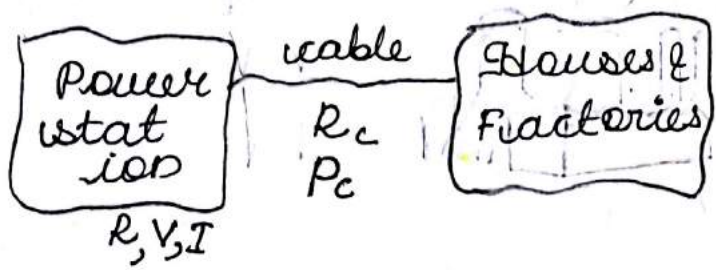

$$P = VI$$

$$\therefore I = \frac{P}{V}$$

Power dissipation in cable

$$P_c = I^2 R_c$$


$$P_c = \left(\frac{P^2}{V^2}\right) R_c$$

$$P_c \propto \frac{1}{V^2}$$

* To reduce power loss increase voltage. If V is very high, it is dangerous, so in the other end step-down transformers are used.

combination of Resistors

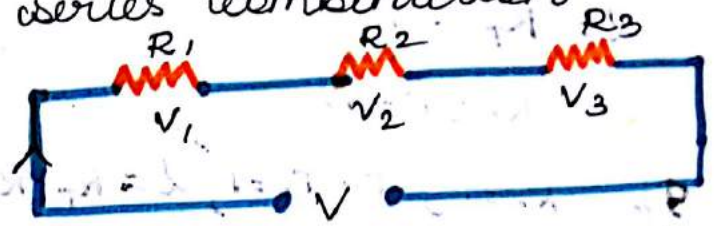* Effective resistance in series combination



In series I constant
 V - ADD'S

$$V = V_1 + V_2 + V_3$$

$$IR = IR_1 + IR_2 + IR_3$$

$$R_s = R_1 + R_2 + R_3$$


$$V = IR$$

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

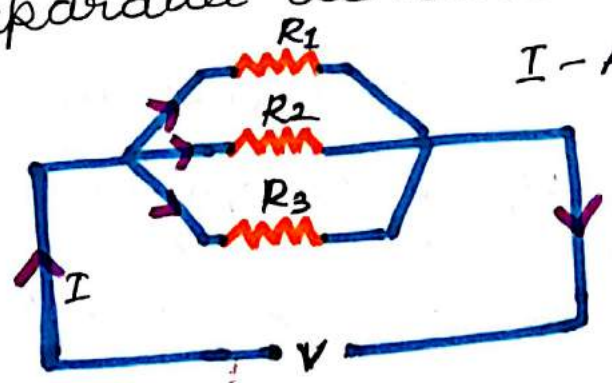* Effective resistance in parallel combination



I - ADD'S

In parallel V - const

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V = IR$$

$$I = \frac{V}{R}$$


$$I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

Similar

CELL

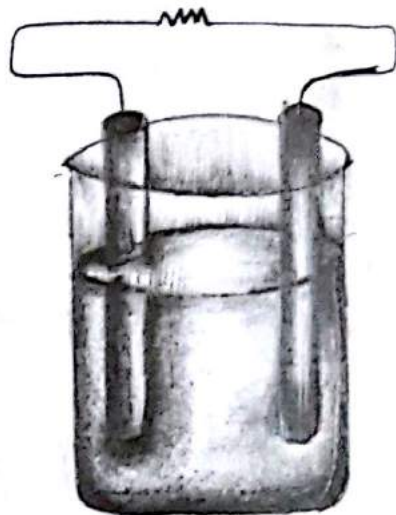

An electric cell is a device which converts chemical energy into electrical energy.

Internal resistance of a cell (r)

It is the resistance offered by the cell when current flows through it.


* Factors affecting Internal resistance

- (1) Distance b/w the plates
- (2) Nature of electrolyte
- (3) Nature of electrodes
- (4) Area of electrodes.
- (5) Temperature of the solution
- (6) External resistance.

Terminal Potential difference (V)

Is the potential difference between the terminals of a

-5-
cell in a closed circuit.

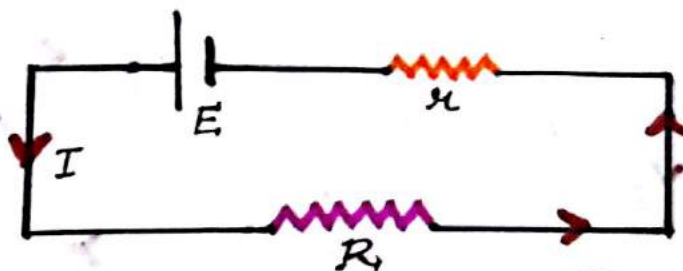

consider a cell of EMF E and internal resistance r connected to an external resistance ' R '.

$$I = \frac{V}{R}$$

$$I = \frac{E}{R+r}$$

$$I = \frac{\text{Total emf}}{\text{Total resistance}}$$

$$I = \frac{E}{R+r} \dots \textcircled{a}$$

$$E = I(R+r) = IR + Ir \dots \textcircled{1}$$

$$\text{Terminal P.d (V)} = IR$$

$$\therefore \textcircled{1} \Rightarrow E = V + Ir$$

$$\therefore V = E - Ir$$

$$V = IR \dots \textcircled{b}$$

$$\textcircled{a} \text{ in } \textcircled{b} \Rightarrow V = \left(\frac{E}{R+r} \right) R$$

$$V = \frac{ER}{R+r}$$

$$V = E - Ir \text{ (when } I=0, r=0)$$


$$V = E - 0 \times 0$$

$$V = E \therefore \text{Terminal p.d} = \text{emf}$$

Combination of cells in series.

consider a number of cells of emf's $E_1, E_2, E_3, \dots, E_n$ of internal resistances $r_1, r_2, r_3, \dots, r_n$.

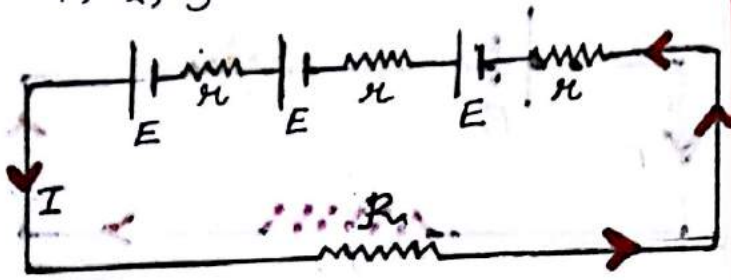$I \rightarrow$ current
 $V_1, V_2, V_3 \dots V_n$ terminal p.d.s



$$I = \frac{\text{Total emf.}}{\text{Total resistance}}$$

$$I = \frac{nE}{nr + R}$$

$$I(nr + R) = nE$$

$$nrI + IR = nE$$

$$nrI = nE - IR$$


$$r = \frac{nE - IR}{nI}$$

$$r = \frac{E}{I} - \frac{R}{n}$$

* $E_{eq} = E_1 + E_2 + E_3 + \dots + E_n$

* $r_{eq} = r_1 + r_2 + r_3 + \dots + r_n$

cells in parallel

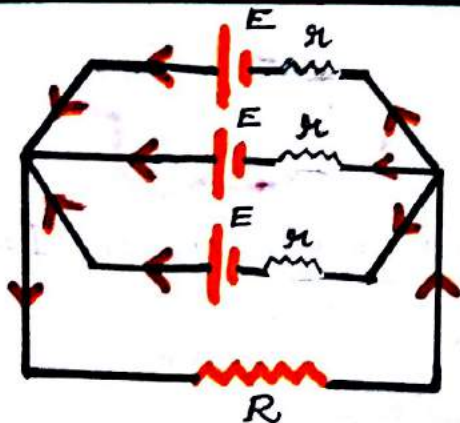

$$I = \frac{\text{Total emf.}}{\text{Total resistance}}$$

$$I = \frac{E}{\frac{r}{n} + R}$$

$$I = \frac{E}{\frac{nr + R}{n}}$$

$$I = \frac{E}{\frac{nr + R}{n}}$$

$$I = \frac{nE}{nr + R}$$

$$I(nr + R) = nE$$

$$Inr + nRI = nE$$

$$Inr = nE - nRI$$


$$r = \frac{nE}{I} - \frac{nRI}{I}$$

$$r = \frac{nE}{I} - nR$$

* $\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots + \frac{1}{r_n}$

* $E_{eq} = r_{eq} \left[\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3} + \dots + \frac{E_n}{r_n} \right]$
 $E_1, E_2 \dots E_n$ etc are cells.

mixed grouping

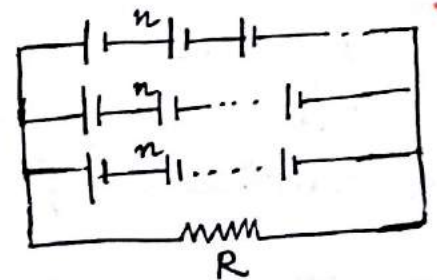

$$i = \frac{nE}{\frac{nr}{m} + R} = \frac{nmE}{nr + mR}$$

$$i = \frac{nmE}{nr + mR}$$

n-cells no
m-rows


Similar

Kirchoff's law's

Kirchoff's first Law (Junction rule)

Algebraic sum of currents meeting at any junction is equal to zero.

$$\sum i = 0$$

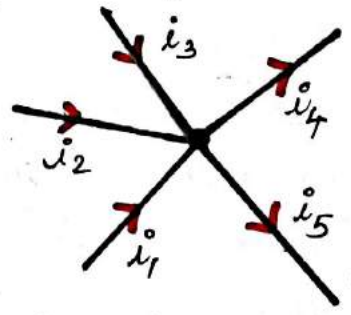

i_2 from fig


$$i_1 + i_2 + i_3 - i_4 - i_5 = 0$$

$$\therefore i_1 + i_2 + i_3 = i_4 + i_5$$

Kirchoff's second law (Loop rule)

The Algebraic sum of product of current and resistance in a loop is equal to the algebraic sum of emf's in that loop.

$$\sum iR = \sum E$$

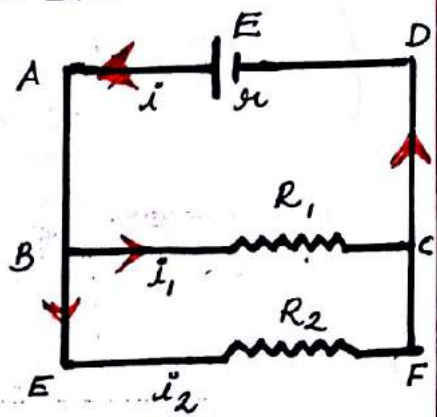

- mesh ABCDA $i_1 R_1 + i r = E$
- mesh BEFCB $i_2 R_2 - i_1 R_1 = 0$
- mesh AEFDA $i_2 R_2 + i r = E$


Wheatstone's Bridge

Wheatstone's principle

In the balanced condition, when $i_g = 0$,

$$\frac{P}{Q} = \frac{R}{S}$$

Wheatstone's Network

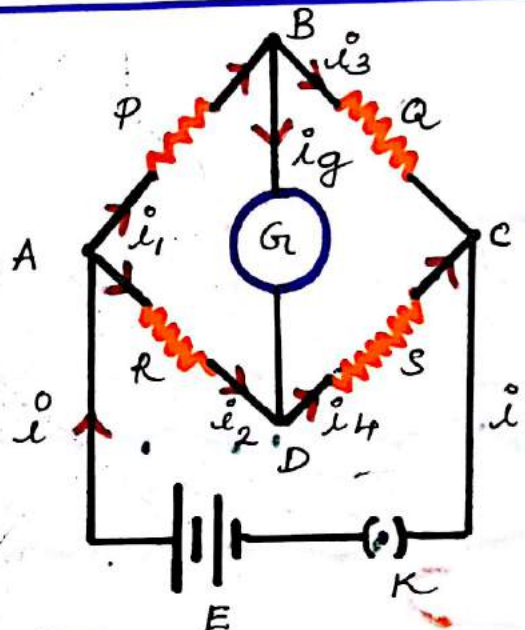

at junction B (1st rule)

$$i_1 = i_g + i_3$$

$$i_g = 0$$

$$\therefore i_1 = i_3 \quad \text{--- (1)}$$

at junction D (1st rule)

$$i_2 + i_g = i_4 \quad (i_g = 0)$$

$$\therefore i_2 = i_4 \quad \text{--- (2)}$$

Applying Kirchoff's IInd law in ABDA & BCDB

(i) loop/Mesh ABDA

$$i_1 P + i_g G - i_2 R = 0 \quad (i_g = 0)$$

$$\therefore i_1 P = i_2 R \quad \text{--- (3)}$$

loop BCDB

$$i_3 Q - i_4 S - i_g G = 0$$

$$i_3 Q = i_4 S \dots (4) \quad i_g = 0$$

$$(3) \div (4)$$


$$\frac{i_1 P}{i_3 Q} = \frac{i_2 R}{i_4 S} \dots (5)$$

substituting (1) & (2) in (5)

$$\frac{P}{Q} = \frac{R}{S} \quad \text{when } i_g = 0$$

METRE BRIDGE.

circuit

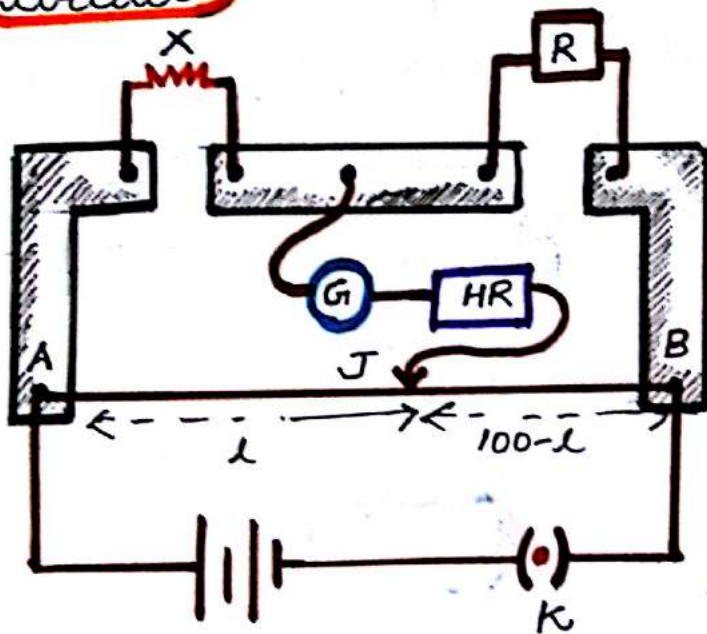

principle

wheatstone bridge principle is the principle of metre bridge. In a balanced condition when $i_g = 0$,

$$\frac{P}{Q} = \frac{R}{S}$$

connections are made as shown in the figure. unknown resistance x is connected in one gap (left & right). known resistance R in other gap. Move the jockey until you get null deflection in galvanometer G . Measure balancing length l ($= AJ$)
 $\therefore BJ = 100 - l$.

According to wheatstone's principle

$$\frac{P}{Q} = \frac{R}{S}$$

$$AJ = l, \quad BJ = 100 - l$$

$$\therefore \frac{X}{R} = \frac{l}{100 - l}$$

$$X = R \left(\frac{l}{100 - l} \right)$$

Thus unknown resistance ' x ' can be calculated by using metre bridge

* $\rho \rightarrow$ Resistance / unit length

$$\rho = \frac{X \pi r^2}{l}$$

* specific resistance ρ can be calculated by measuring ' x ' and ' l '

Similar

POTENTIOMETER

It is a device used to measure potential difference. It consists of a uniform resistance wire usually 10m long stretched on a wooden board in zigzag manner.

comparing emf of primary cells using potentiometer.

principle of potentiometer

$$V \propto l$$

where I, ρ and A - constants


potential difference (V) across any length (l) of wire is directly proportional to the length when constant current (I) flows through a wire of uniform area of cross section (A) and resistivity (ρ).

circuit & procedure.

* make connections as shows below with 2 primary cells of emf's E_1 and E_2 .

* According to principle of potentiometer
 $E \propto l$
 $E = k.l$

circuit

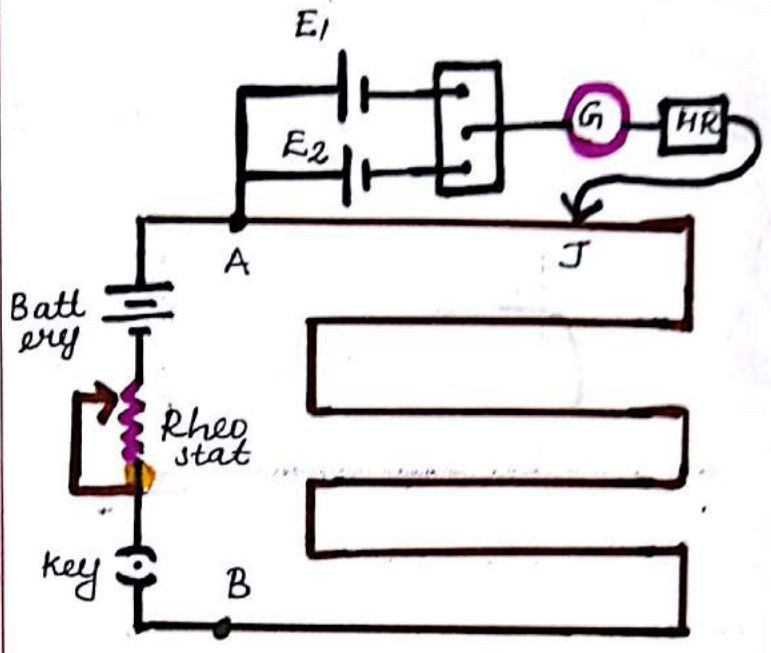

* Include the E_1 alone in the circuit and measure balancing length l_1

$$E_1 = k.l_1 \dots \dots \textcircled{1}$$

* Include E_2 alone in the circuit and measure balancing length l_2

$$E_2 = k.l_2 \dots \dots \textcircled{2}$$

$$\textcircled{1} \div \textcircled{2}$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

using this formula emf's of two cells can be compared.

Internal Resistance of a cell - using potentiometer.

make the connections as shows be-

law using a cell of emf E and external resistance R .

* with k_2 - open measure balancing length.

$$E \propto l_1$$

$$E = k l_1 \quad \dots \text{--- (1)}$$

* close k_2 , measure balancing length

$$V \propto l_2$$

$$\frac{ER}{R+r} \propto l_2$$

$$\frac{ER}{R+r} = k l_2 \quad \dots \text{--- (2)}$$

$$\text{(1) } \div \text{(2)} \Rightarrow \frac{E}{\frac{ER}{R+r}} = \frac{l_1}{l_2}$$

$$\frac{R+r}{R} = \frac{l_1}{l_2}$$

$$1 + \frac{r}{R} = \frac{l_1}{l_2}$$

$$\frac{r}{R} = \frac{l_1}{l_2} - 1$$

$$\frac{r}{R} = \frac{l_1 - l_2}{l_2}$$

$$r = R \left(\frac{l_1 - l_2}{l_2} \right)$$

By knowing the values of

R, l_1, l_2, r can be calculated

